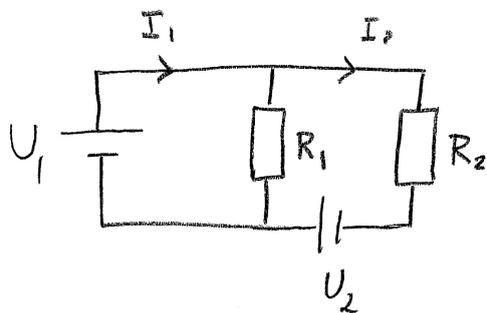


1



LF til kontinuasjons-
eksamen vå 2010.

LF er knapt og
ufullstendig.

$$a) \quad U_1 + U_2 = R_2 \cdot I_2$$

$$I_2 = \frac{U_1 + U_2}{R_2} = \frac{13 \text{ V}}{50 \Omega} = \underline{\underline{0.26 \text{ A}}}$$

$$b) \quad (I_1 - I_2) R_1 = U_1$$

$$I_1 = I_2 + \frac{U_1}{R_1} = \frac{U_1 + U_2}{R_2} + \frac{U_1}{R_1}$$

$$I_1 - I_2 = \frac{U_1}{R_1} = \underline{\underline{0.04 \text{ A}}} = \frac{R_1(U_1 + U_2) + R_2 U_1}{R_1 R_2}$$

$$= \frac{100 \cdot 13 + 50 \cdot 4}{50 \cdot 100}$$

$$I_1 = \frac{1500}{50 \cdot 100} = \underline{\underline{0.30 \text{ A}}}$$

Så strømmen gjennom motstand R_1 er 0.04 A

2

$$a) \quad R = \frac{\rho \cdot L}{A} \quad \text{så} \quad A = \frac{\rho \cdot L}{R}$$

$$A = \frac{2.65 \cdot 10^{-8} \cdot 10^5 \text{ m}}{500 \Omega} = 5.3 \cdot 10^{-8+5-3} \text{ m}^2$$

$$= 5.3 \cdot 10^{-6} \text{ m}^2 = \underline{\underline{5.3 \text{ mm}^2}}$$

b) Strøm gjennom ledning


$$I \cdot U = P, \quad I = \frac{P}{U} = \underline{\underline{3 \text{ A}}}$$

Spennning over strømledningen: $R \cdot I = R \cdot P/U$

$$\text{Effekttap er } R \cdot P/U \cdot P/U = R \cdot P^2/U^2$$

$$\text{Effekttap/Effekt} = \frac{R P^2/U^2}{P} = \frac{R \cdot P}{U^2} = \frac{500 \cdot 3000 \text{ k}}{1000^2 \text{ k}^2} = 1.5 \cdot 10^{-3} = \underline{\underline{0.15\%}}$$

3.

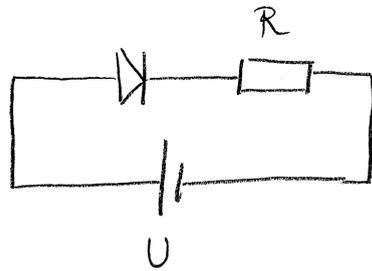

$$I = I_0 (e^{U/U_T} - 1)$$

$$I \cdot R = U_R$$

$$U_R = I \cdot R$$

$$U_d = U_T \ln \left(1 + \frac{I}{I_0} \right)$$

$$U = I \cdot R + U_T \ln \left(1 + \frac{I}{I_0} \right)$$

numerisk finner vi at:

$$I \cdot 2000 + 0.026 \ln(I \cdot 10^8) = 2.0V \quad \text{gir}$$

$$\Rightarrow I = \underline{\underline{0.85 \text{ mA}}}$$

Forklar.